

T4D08 (A)

What is the voltage across the resistor if a current of 1 ampere flows through a 10 ohm resistor?

- A. 10 volts**
- B. 1 volt
- C. 11 volts
- D. 9 volts

T4D09 (A)

What is the voltage across the resistor if a current of 2 amperes flows through a 10 ohm resistor?

- A. 20 volts**
- B. 0.2 volts
- C. 12 volts
- D. 8 volts

T4D10 (C)

What is the current flowing through a 100 ohm resistor connected across 200 volts?

- A. 20,000 amperes
- B. 0.5 amperes
- C. 2 amperes**
- D. 100 amperes

T4D11 (C)

What is the current flowing through a 24 ohm resistor connected across 240 volts?

- A. 24,000 amperes
- B. 0.1 amperes
- C. 10 amperes**
- D. 216 amperes

T4E01 (D)

What unit is used to describe electrical power?

- A. Ohm
- B. Farad
- C. Volt
- D. Watt**

T4E02 (A)

What is the formula used to calculate electrical power in a DC circuit?

- A. Power (P) equals voltage (E) multiplied by current (I)**
- B. Power (P) equals voltage (E) divided by current (I)
- C. Power (P) equals voltage (E) minus current (I)
- D. Power (P) equals voltage (E) plus current (I)